

For the below circuit, determine the equivalent resistance seen between points A and B.

