

For the given circuit, use the principle of superposition to find I_0 . Show the steps of your work.

