

For the given circuit:

1. Find I_y
2. Find R_x
3. Calculate the power of the unknown element. State whether the power is absorbed or delivered by the unknown element.

