

For the circuit below use the node voltage method to generate a solvable system of equations for the circuit/ You do not have to solve the generated system of equations.

