


Practice Quiz Seven: RLC Circuit Analysis under DC Conditions (Easy)

For the RLC circuit at steady state shown below, find the following:


- a) v_1
- b) v_2
- c) i_1
- d) i_2

Finally, find the energy stored in both the inductor and the capacitor.


Suggested time limit: 10 minutes

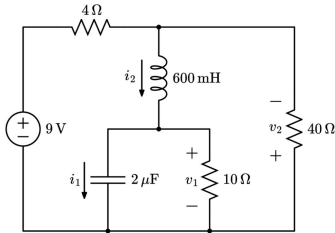

Steady State Conditions

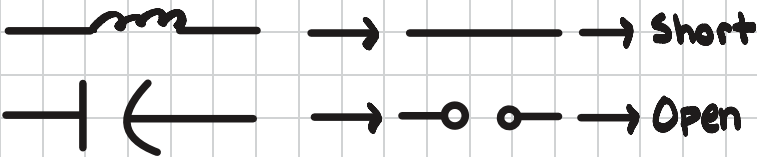


Step #1 Redraw Circuit

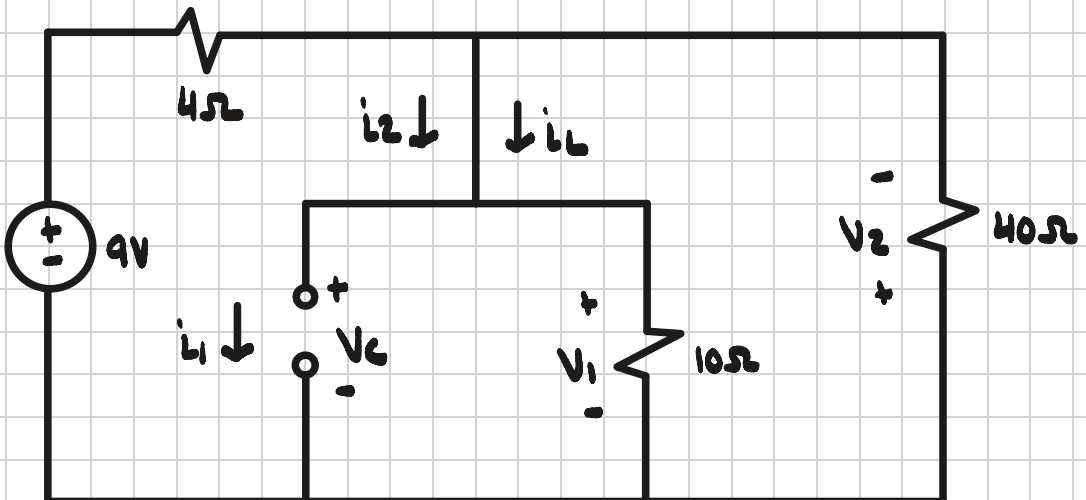

Step #2 Find i_1


$$i_1 = 0A$$

Step #3 Redraw Circuit

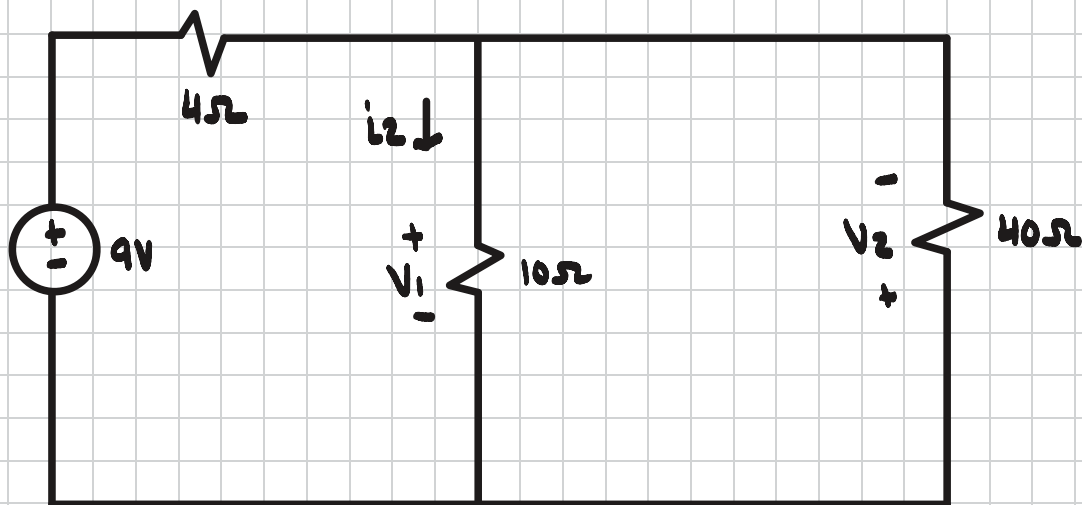

Step #4 Find V_1
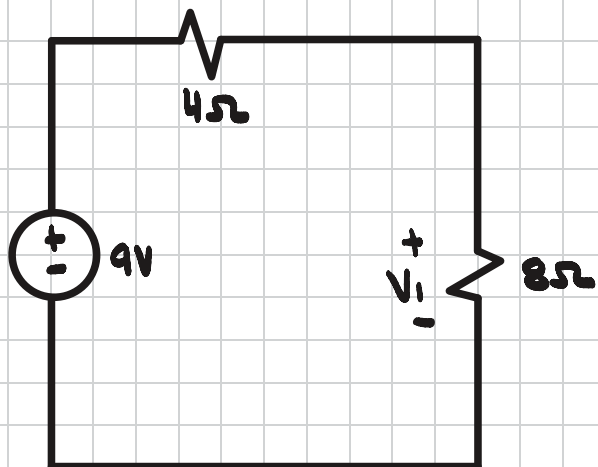
$$\left(\frac{1}{40} + \frac{1}{10}\right)^{-1} = 8\Omega$$




$$V_1 = 9 \left(\frac{8}{8+4} \right)$$

$$V_1 = 6V = V_2$$

Step # 5 Find V_2

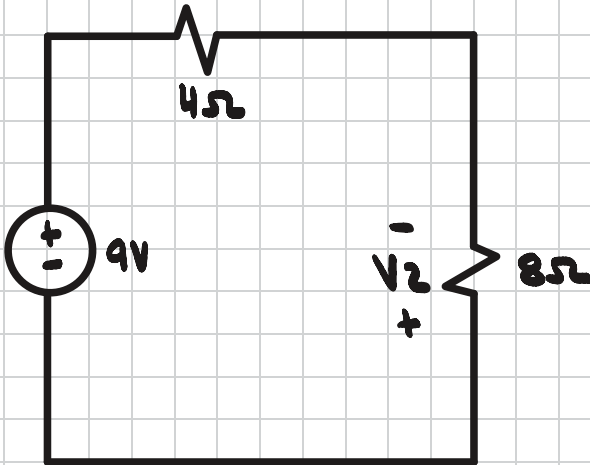
$$\left(\frac{1}{40} + \frac{1}{10}\right)^{-1} = 8\Omega$$



$$V_2 = -9\left(\frac{8}{8+4}\right)$$

$$V_2 = -6V$$

Step # 6 Find i_2

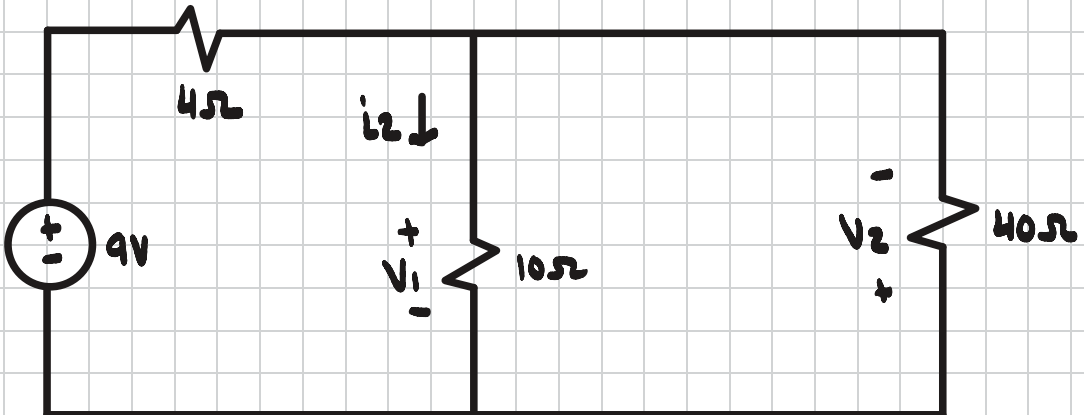

$$i_2 = \frac{V_1}{10} = \frac{6}{10}$$

$$i_2 = 600mA = i_L$$

Step # 7 Find Energy

$$W_{\text{capacitor}} = \frac{1}{2} CV^2 = \frac{1}{2} (2 \cdot 10^{-6}) (6)^2$$

$$W_{\text{capacitor}} = 36 \mu\text{J}$$

$$W_{\text{inductor}} = \frac{1}{2} Li^2 = \frac{1}{2} (600 \cdot 10^{-3}) (600 \cdot 10^{-3})^2$$

$$W_{\text{inductor}} = 0.108 \text{ J}$$