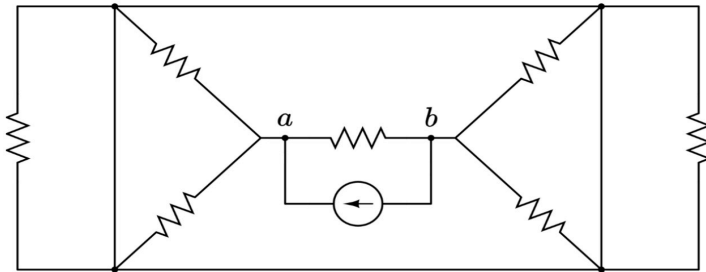


Practice Quiz Two: Equivalent Resistance (Hard)


For the circuit shown below, where every resistor has an identical resistance R , find the equivalent resistance R_{ab} seen by the independent current source. Express your answer in terms of R .

Suggested time limit: 15 minutes




I will use label like R_1 and R_2
so you know which resistor I am referring
to but all have a value of R

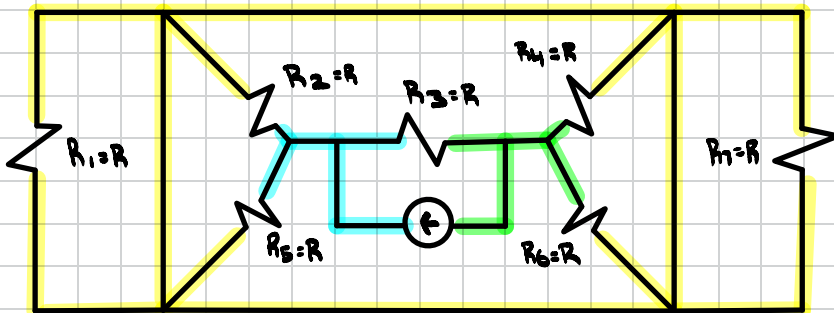Start by labeling nodes which are
wires between at least two components



Cyan = Node A
Green = Node B
Yellow = Node C

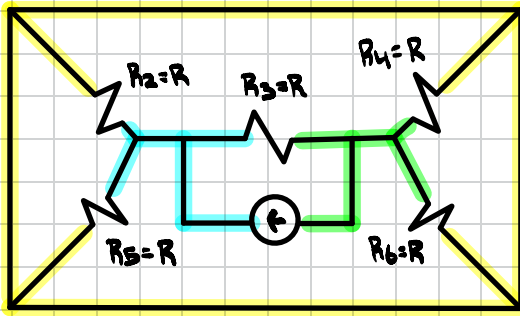
R_1 and R_7 will short because
both ends are connected by
the same node so you can
remove them from the circuit



Cyan = Node A
Green = Node B
Yellow = Node C

R_2 and R_5 are in parallel because both ends of the resistors are connected by same node (Node A and C)

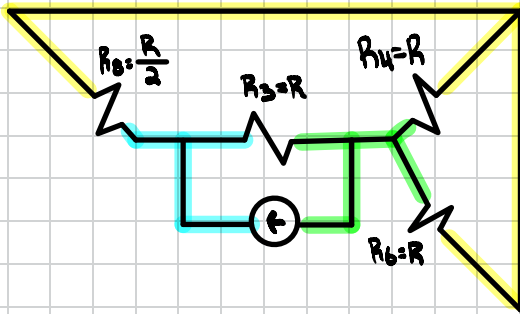
$$\left(\frac{1}{R} + \frac{1}{R}\right)^{-1} = \frac{R}{2}$$



Cyan = Node A
Green = Node B
Yellow = Node C

R_4 and R_6 are in parallel for the same reason (Node B and C)

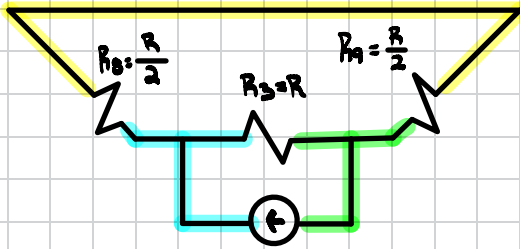
$$\left(\frac{1}{R} + \frac{1}{R}\right)^{-1} = \frac{R}{2}$$



Cyan = Node A
Green = Node B
Yellow = Node C

R_8 and R_9 are in series
because the same current
goes through it


$$\frac{R}{2} + \frac{R}{2} = R$$

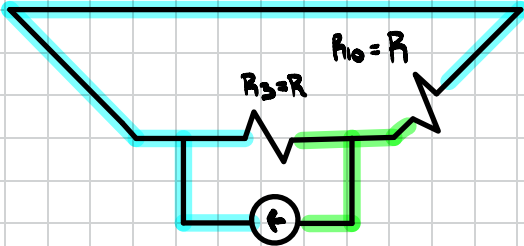

Cyan = Node A
Green = Node B

R_{10} and R_3 are in parallel
Since they share the same
nodes (Node A and B)
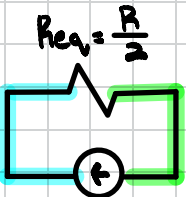
$$\left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = \frac{R}{2}$$



Cyan = Node A
Green = Node B