

Linear Circuits One (EEL 3004C)

Practice Exam 2 Solutions

Kevin Ho

Christian Keplinger


Hunter Volonino

Practice Exam 2 Q1 Solution

Friday, October 17, 2025 7:25 PM

For the given circuit, use nodal analysis to find the following:

- Every single node voltage
- I_o

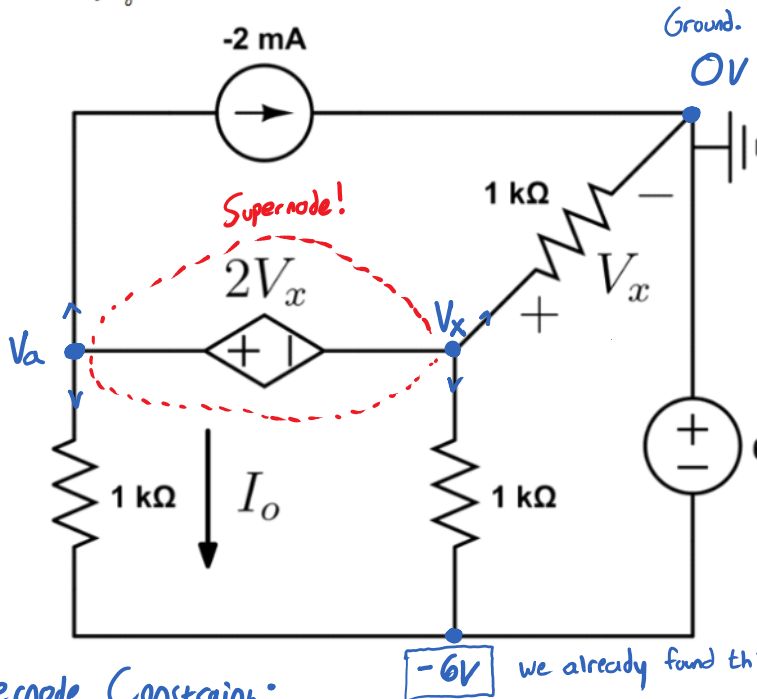

* V_x is the voltage difference between its node (V_x) and ground.

* We don't need to do a KCL at the -6V node because its voltage is given by the source (it is 0-6V, so -6V, due to flipped polarity).

Supernode Constraint:

$$V_a - V_x = 2V_x$$

Simplify:

$$V_a - 3V_x = 0$$

Matrix:

$$\begin{bmatrix} 1 & -3 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} V_a \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ -10 \end{bmatrix}$$

so,

$$\begin{bmatrix} V_a = -6V. \\ V_x = -2V. \end{bmatrix}$$

$$i_o = \frac{V_a + 6}{1000}$$

$$i_o = \frac{-6 + 6}{1000} = \frac{0}{1000} = 0A.$$

so,

$$i_o = 0A.$$

KCL @ V_a and V_x Supernode:

$$-0.002 + \frac{V_a + 6}{1000} + \frac{V_x}{1000} + \frac{V_x + 6}{1000} = 0.$$

Simplify:

this is i_o !

$$1000 \left(-0.002 + \frac{V_a + 6}{1000} + \frac{V_x}{1000} + \frac{V_x + 6}{1000} \right) = 0.$$


$$-2 + V_a + 6 + V_x + V_x + 6 = 0.$$

$$-2 + V_a + 6 + 2V_x + 6 = 0$$

$$V_a + 2V_x + 10 = 0$$

$$V_a + 2V_x = -10.$$

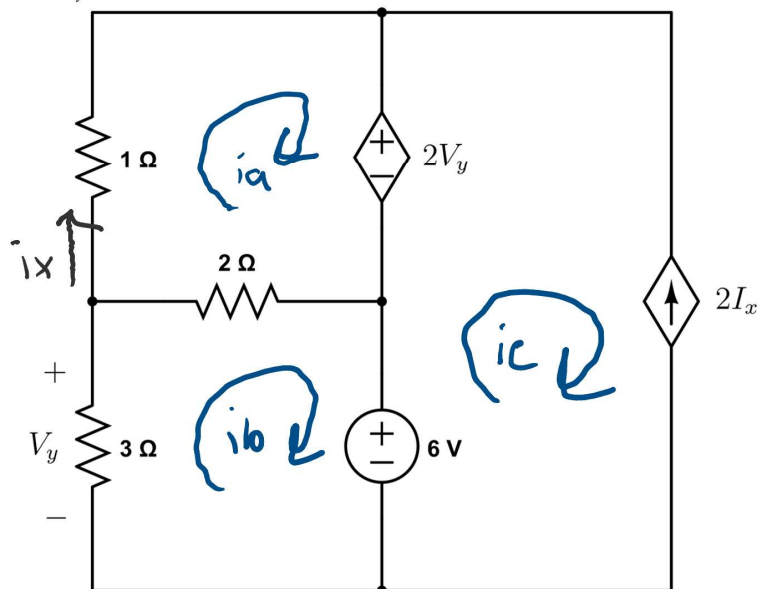For the given circuit, use mesh analysis to find the following:
a) Every single mesh current (assume clockwise direction)
b) V_y



5 unknowns, 5 equations

1. $i_x = i_a$
2. $V_y = -3i_b$, $2V_y = -6i_b$
3. $i_c = -2I_x = -2i_a$

Mesh i_b : $3i_b + 2(i_b - i_a) + 6 = 0$
Simplify $\rightarrow$ $-2i_a + 5i_b = -6$

Mesh i_a : $i_a + 2V_y + 2(i_a - i_b) = 0$
 $\rightarrow i_a - 6i_b + 2i_a - 2i_b = 0$
 $\rightarrow 3i_a - 8i_b = 0$

Solve for i_a, i_b :


$$\begin{bmatrix} -2 & 5 \\ 3 & -8 \end{bmatrix}^{-1} \cdot \begin{bmatrix} -6 \\ 0 \end{bmatrix} = \begin{bmatrix} i_a \\ i_b \end{bmatrix} = \begin{bmatrix} 48A \\ 18A \end{bmatrix}$$

3. $i_c = -2i_a = -96A$

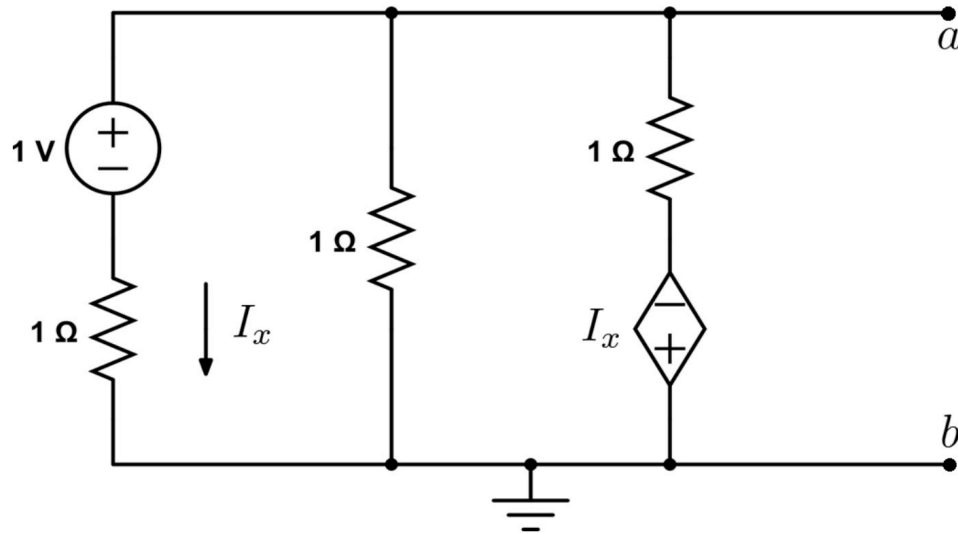
2. $V_y = -3i_b = -54V$

For the given circuit, find the following:

- The Thevenin equivalent circuit seen from a to b
- The Norton equivalent circuit seen from a to b
- The maximum power that could be dissipated in a load resistor R_L connected between a and b



Voc Method

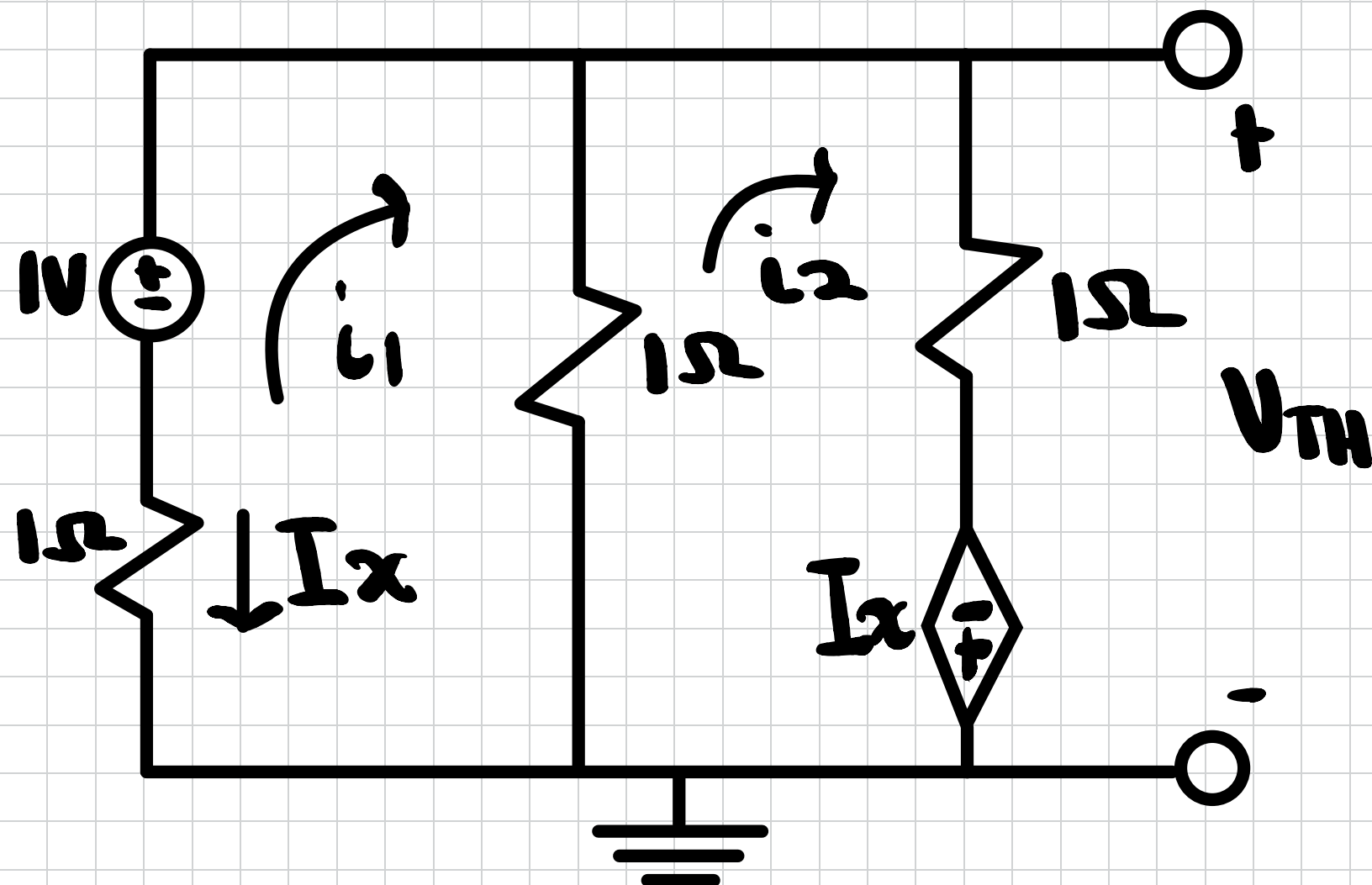

Constraint

$$* i_1 = -I_x$$

Mesh @ i_1

$$1(i_1) - 1 + 1(i_1 - i_2) = 0$$

$$i_1 - 1 + i_1 - i_2 = 0$$

$$2i_1 - i_2 = 1$$

Sub In Constraint

$$2(-I_x) - i_2 = 1$$

$$-2I_x - i_2 = 1 \longrightarrow \text{Eq \# 1}$$

Mesh @ i_2

$$1(i_2 - i_1) + 1(i_2) - I_x = 0$$

$$i_2 - i_1 + i_2 - I_x = 0$$

$$-i_1 + 2i_2 - I_x = 0$$

Sub In Constraint

$$-(-I_x) + i_2 - I_x = 0$$

$$I_x + i_2 - I_x = 0$$

$$i_2 = 0A \longrightarrow \text{Eq \#2}$$

Solve with Both Eq

$$-2I_x - 0 = 1$$

$$I_x = -0.5A$$


KVL @ Rightmost loop

$$I_x + i_2 + V_{TH} = 0$$

$$-0.5 - I(0) + V_{TH} = 0$$

$$V_{TH} = 0.5V$$

Test Voltage Method

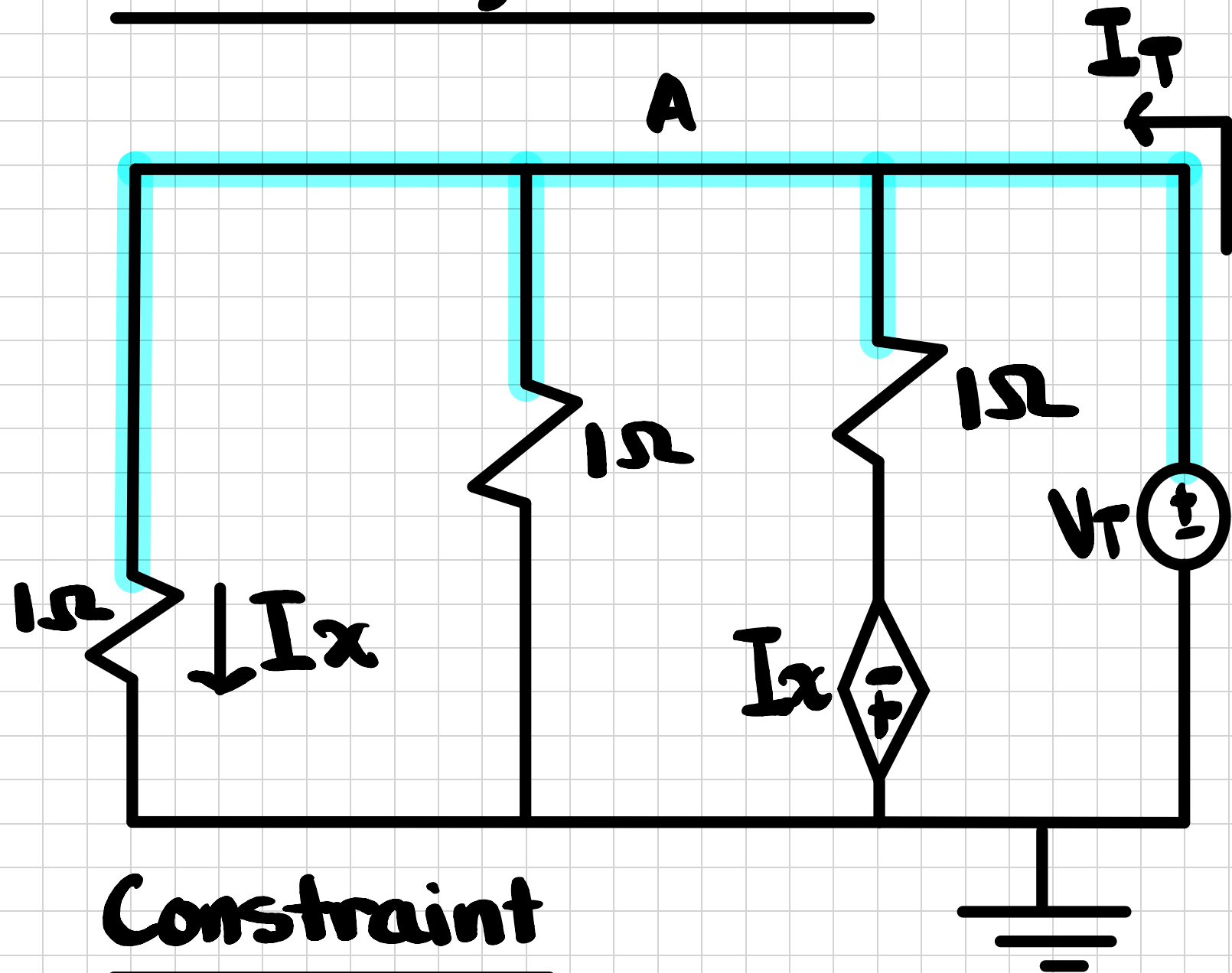

Constraint

$$* I_x = \frac{V_T - 0}{1} = V_T$$

Nodal @ Node A

$$\frac{V_T - 0}{1} + \frac{V_T - 0}{1} + \frac{V_T - (-I_x)}{1} - I_T = 0$$

$$V_T + V_T + V_T + I_x - I_T = 0$$

$$3V_T + I_x - I_T = 0$$

Sub In Constraint

$$3V_T + V_T - I_T = 0$$


$$4V_T = I_T$$

$$\frac{V_T}{I_T} = 0.25 \Omega = \frac{1}{4} \Omega = R_{TH}$$


$$I_{Norton} = \frac{V_{TH}}{R_{TH}}$$

$$I_{\text{Norton}} = \frac{0.5}{0.25} = 2 \text{ A}$$

Thevenin Equivalent

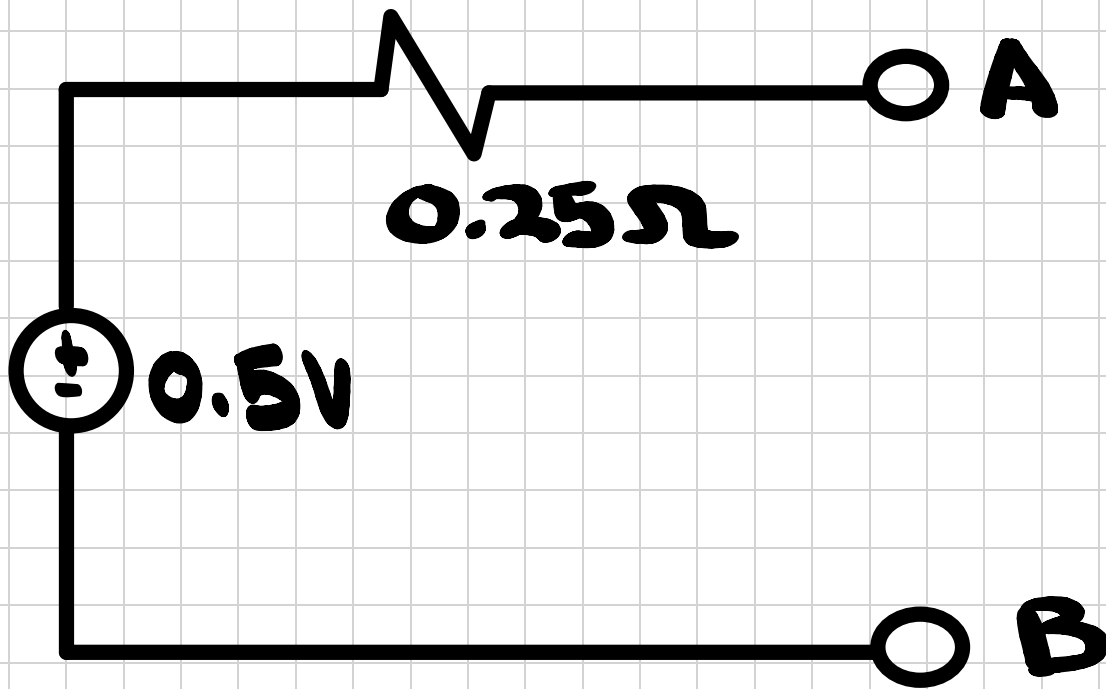

Norton Equivalent

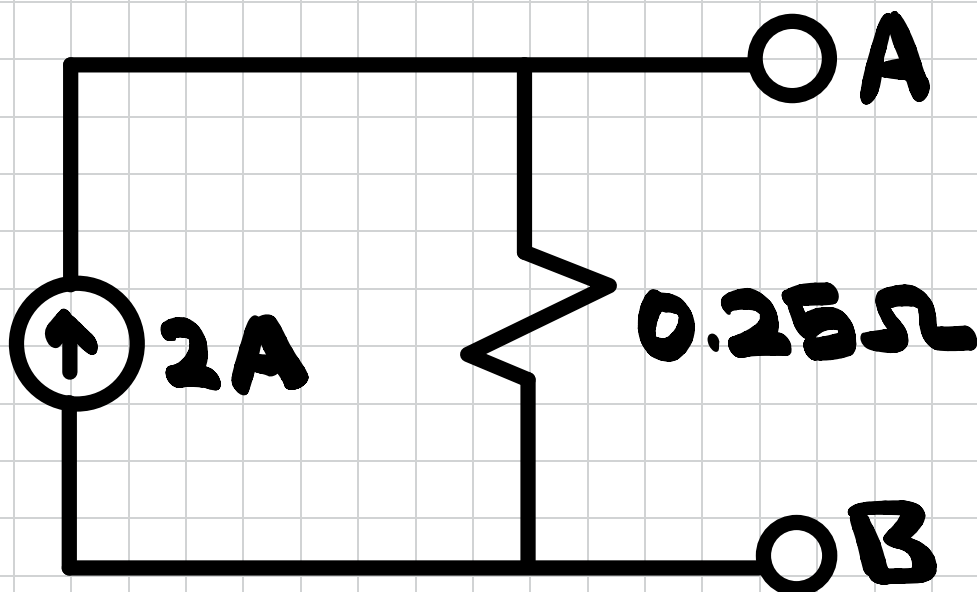

Max Power Transfer

$$P_{\text{MAX}} = \frac{V_{\text{TH}}^2}{4R_{\text{TH}}} = \frac{(0.5)^2}{4(0.25)}$$

$$P_{\text{MAX}} = 0.25 \text{ W}$$