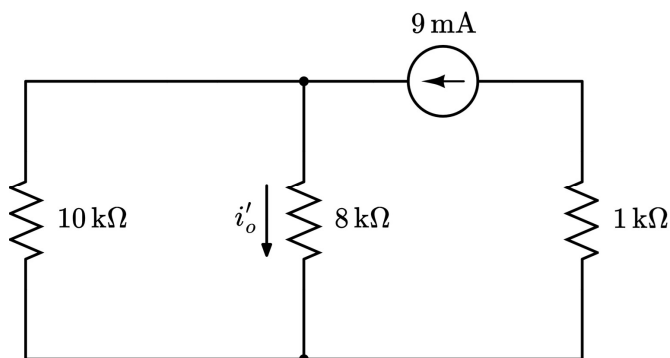


Practice Quiz Three Solution: Superposition (Easy)

For the circuit shown below, use the principle of superposition to find i_o . Clearly redraw the circuit in each state.

Response One: Voltage Source Turned Off (short)



Current Division:


$$i'_o = \underbrace{\frac{10\text{k}\Omega \parallel 8\text{k}\Omega}{8\text{k}\Omega}}_{\text{Unitless Ratio}} \cdot 9\text{mA}$$

The $1\text{k}\Omega$ resistor is not used for current division since the current through it is known.

$$10\text{k}\Omega \parallel 8\text{k}\Omega = \frac{40}{9}\text{k}\Omega$$

$$i'_o = 5\text{A}$$

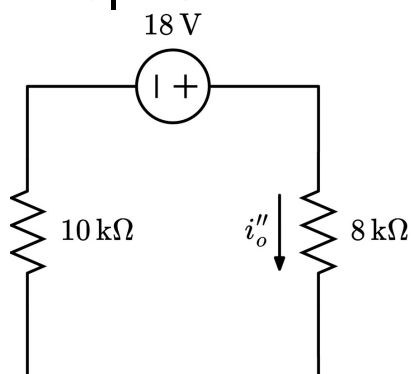Response Two: Current Source Turned Off (open)



Ohm's Law:

$$i''_o = \frac{18\text{V}}{10\text{k}\Omega + 8\text{k}\Omega}$$

$$i''_o = 1\text{mA}$$

Combine Responses: $i_o = i'_o + i''_o = 6\text{mA}$

Self-Grading Rubric	
Clearly redraw the circuit correctly when the voltage source is turned off (Voltage source at 0V is shorted)	+2 points
Clearly redraw the circuit correctly when the current source is turned off (Current source at 0A is open)	+2 points
Correct value for i'_o in response one	+2 points
Correct value for i''_o in response two	+2 points
Correct value for the sum of responses i_o	+2 points