


Linear Circuits One (EEL 3004C)

Practice Exam 3

Matthew Giannacco


For the given circuit, find the following expressions for $t \geq 0$:

- $v_s(t)$
- $i_1(t)$
- $v_1(t)$

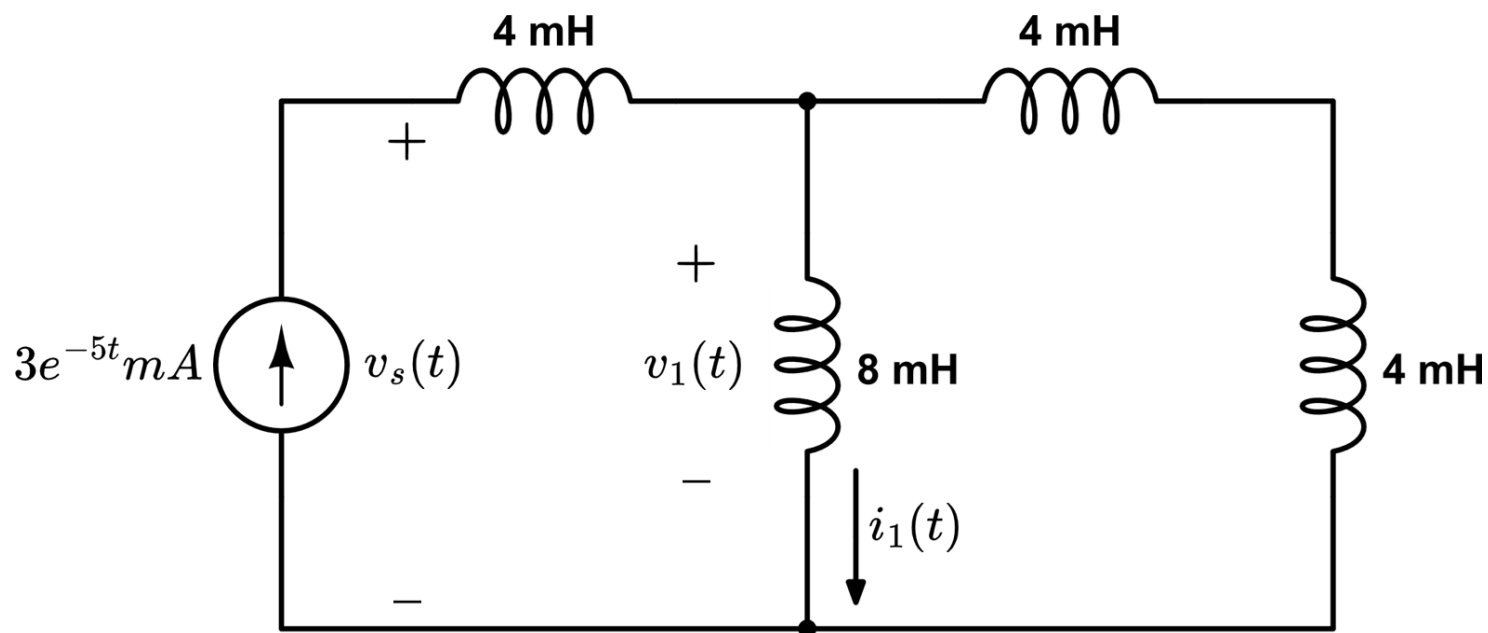

For the given circuit, the switch has been opened for a long time and closes at $t = 0$. Find the following expressions:

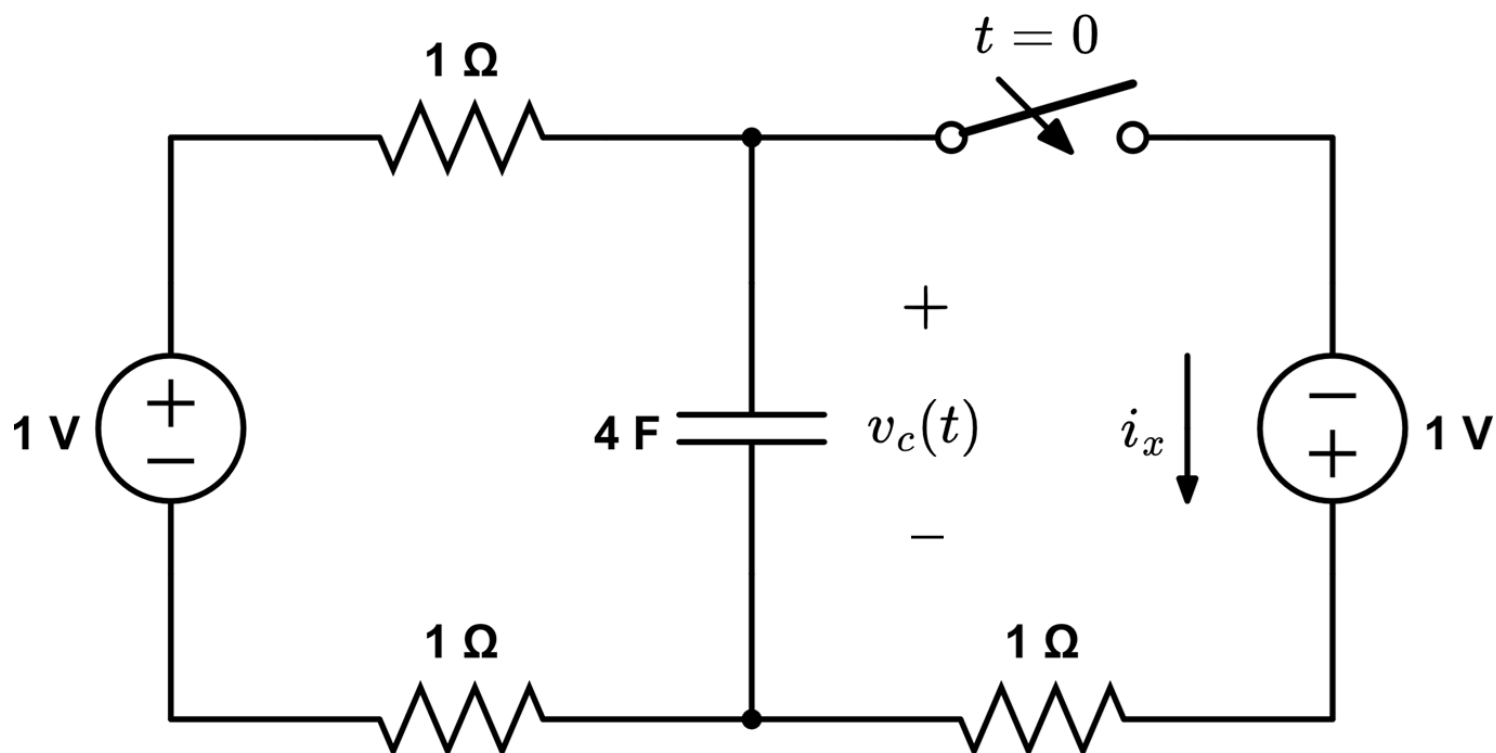- $v_c(0)$
- $v_c(t)$ for $t \geq 0$
- $i_x(t)$ for $t \geq 0$



For the given circuit, the switch has been opened for a long time and closes at $t = 0$. Find the following expressions:

- $i_L(0)$
- $i_L(t)$ for $t \geq 0$
- $i_x(t)$ for $t \geq 0$

