


Linear Circuits One (EEL 3004C)

Practice Exam 1

Matthew Giannacco


For the given circuit, use KVL, KCL, Ohm's Law, and passive sign convention of power to answer the following questions:

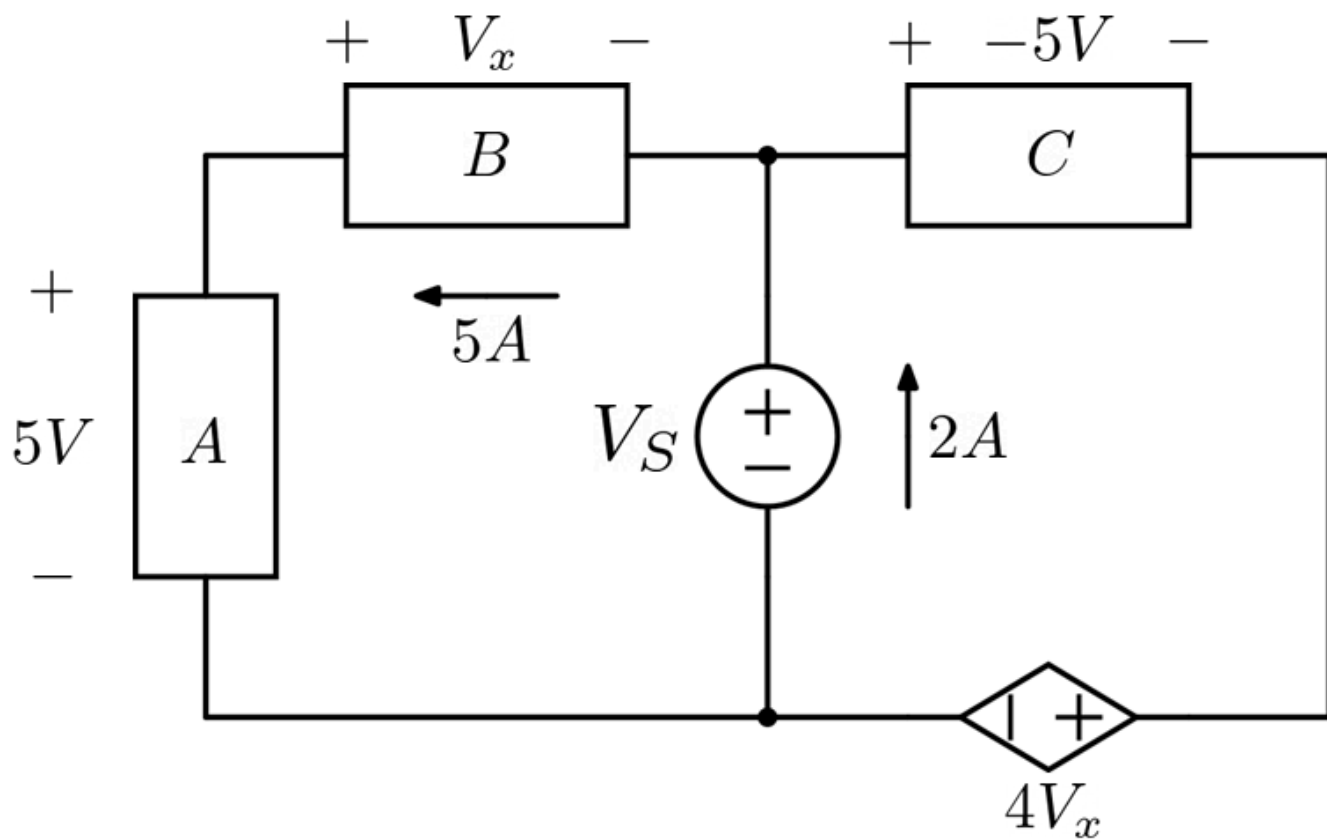- Find V_x
- Find V_s
- Calculate the resistance of circuit element A
- Calculate the power of the dependent source. State whether the power is absorbed or delivered by the dependent source.



For the given circuit, use current division, voltage division, Ohm's Law, and the concept of equivalent resistance to find the following:

- a) V_s
- b) V_1
- c) I_2

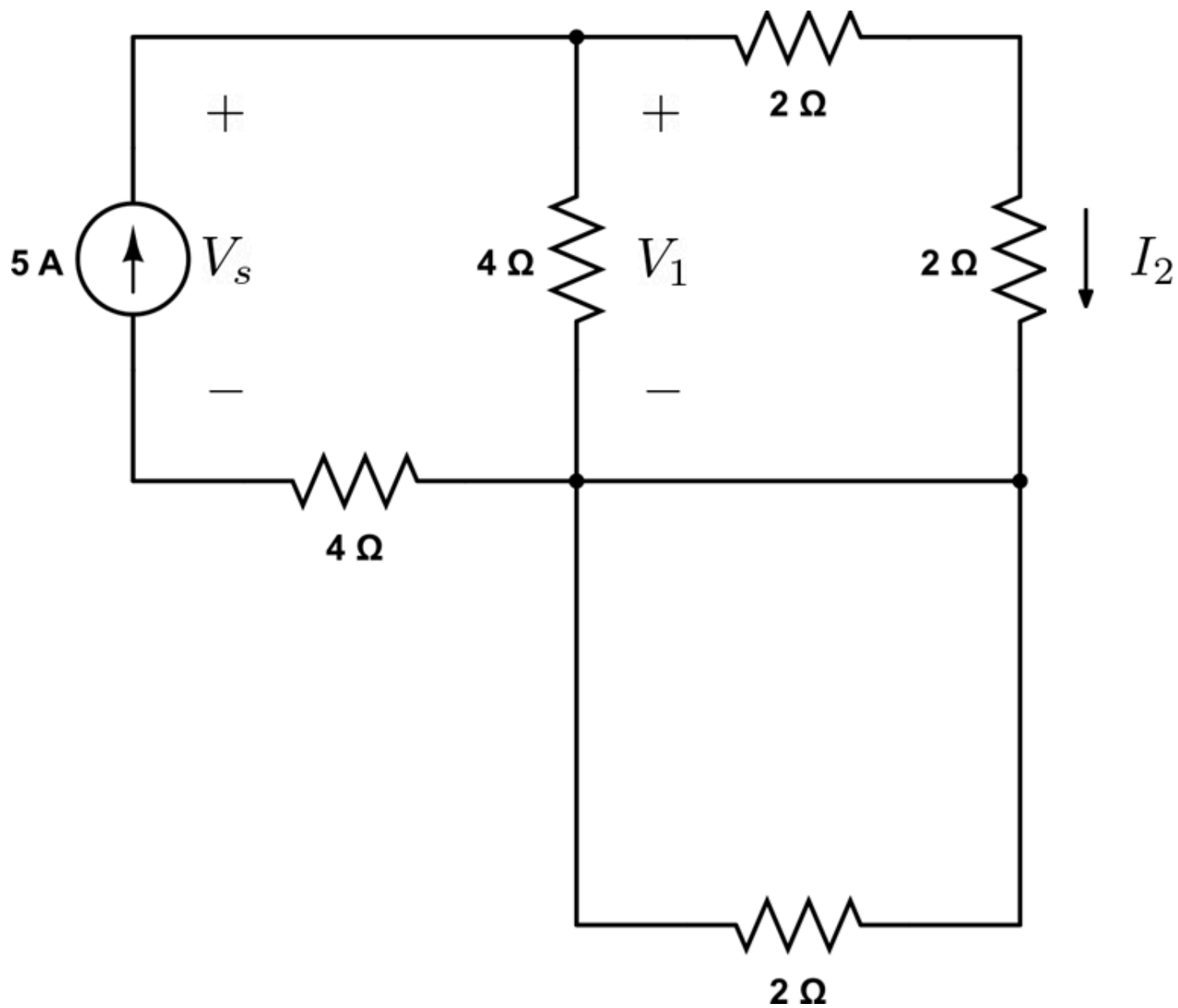

For the circuit below, solve for the equivalent resistance seen by the 1-Volt source (Hint: $R_{eq} = \frac{V_{in}}{I_{in}}$)

