

In the circuit below, determine $i(t)$

