
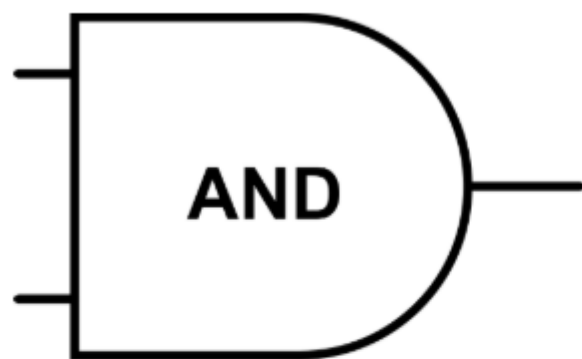


Boolean Algebra Basic Operations


Giannacco

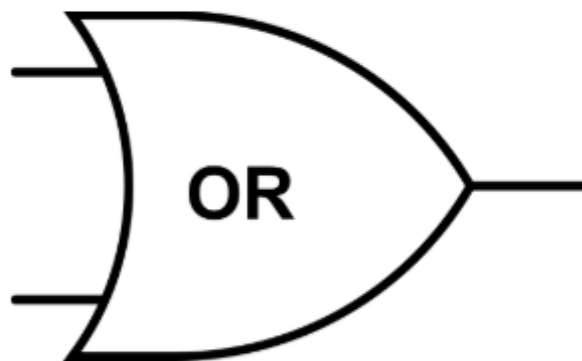

If the input contains a 0,
the output will be 0.



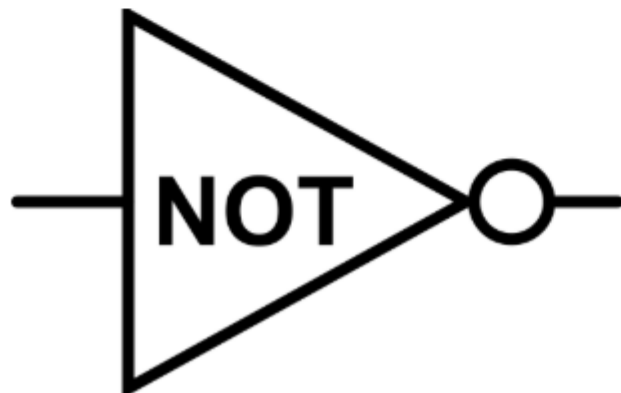If the input contains a 1,
the output will be 1.



The input is flipped
to obtain the output.