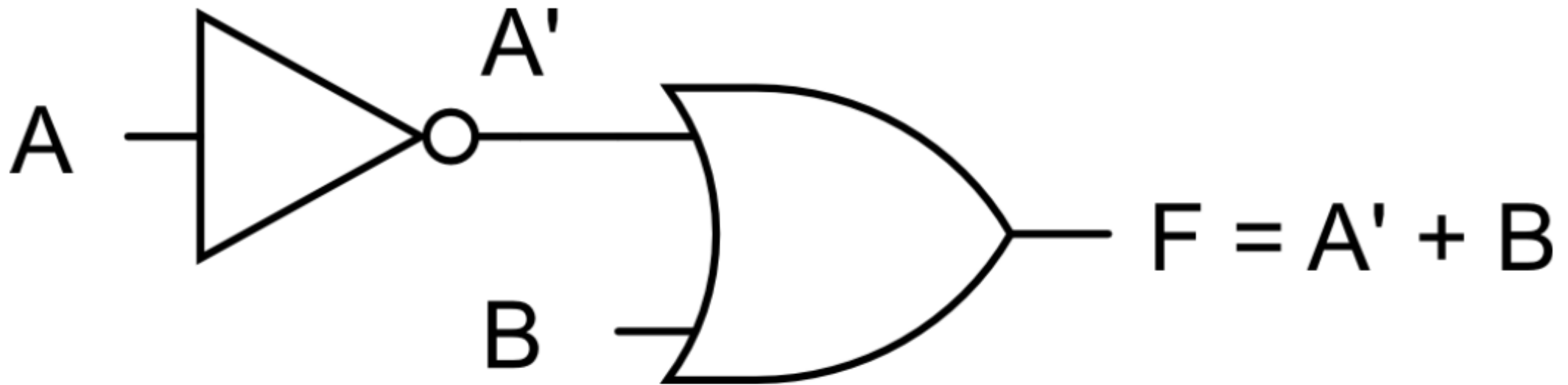


Boolean Expressions

Giannacco

A Boolean algebra expression can be represented using logic gates (and, or, inverse)



We can write a truth table for every function F which includes all possible inputs and corresponding outputs

AB	A'	$F = A' + B$
00	1	1
01	1	1
10	0	0
11	0	1