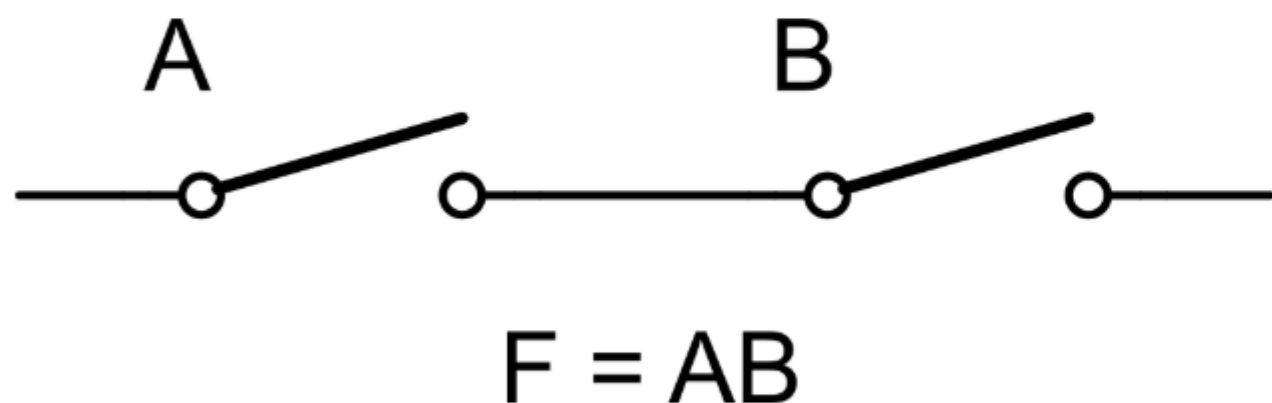



Implementing Functions with Switches

Giannacco

OR Switches



AND Switches

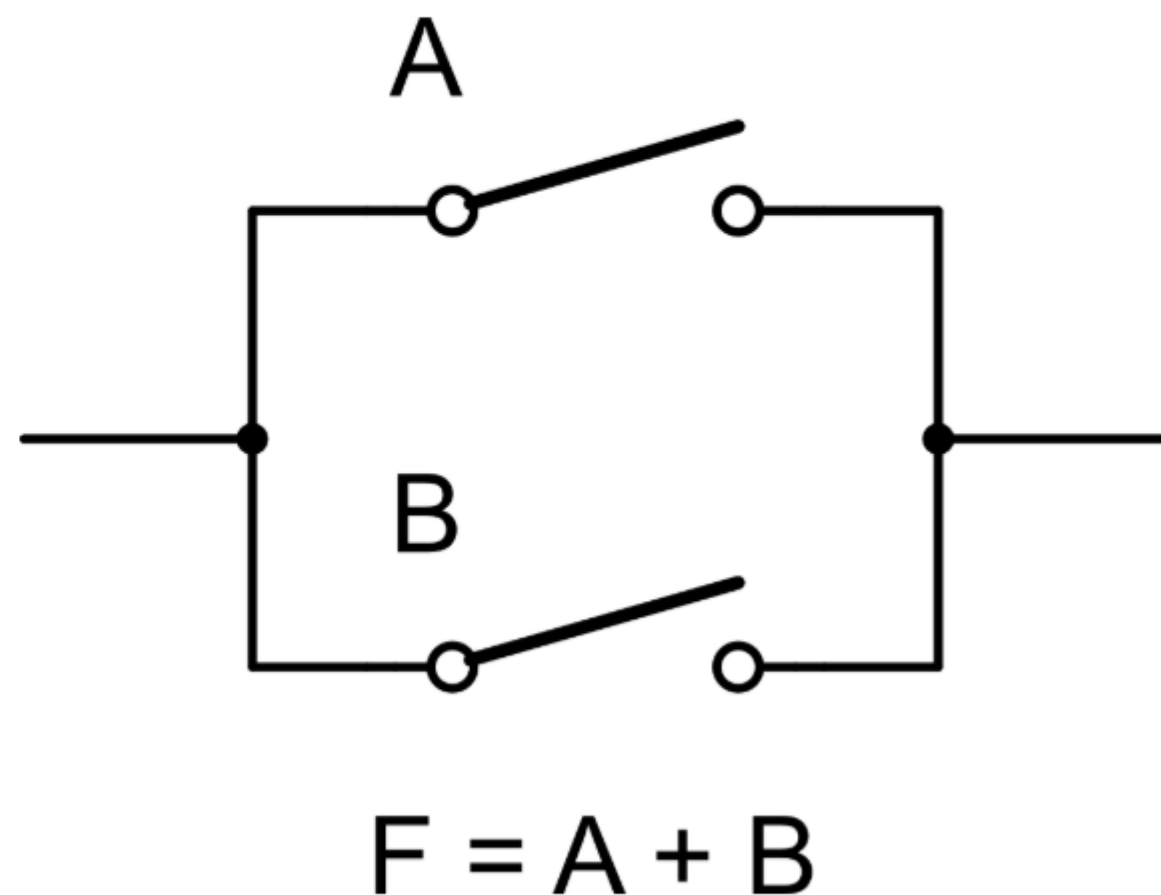

Switches in series will result in a product

Switches in parallel will result in a sum