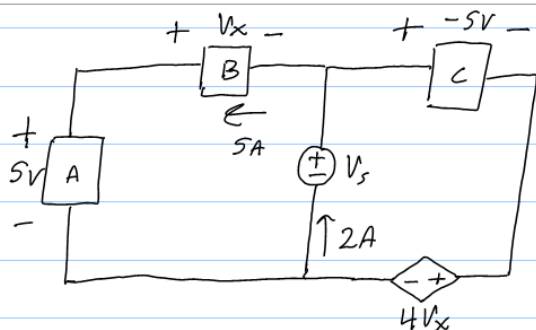


**Linear Circuits One (EEL 3004C)**

**Practice Exam 1 Solutions**

**Matthew Giannacco**

**Hunter Volonino**



Find  $V_x$ ,  $V_s$ , resistance of A,  
power of dependent source.  
Absorbed or delivered?

KVL outer loop:

$$-5 + V_x - 5 + 4V_x = 0$$

$$5V_x = 10$$

$$V_x = 2V$$

KVL left loop:

$$-5 + V_x + V_s = 0$$

$$-5 + 2 + V_s = 0 \quad \leftarrow \text{Substitute } V_x \rightarrow$$

$$-3 + V_s = 0$$

$$V_s = 3V$$

(Or:) KVL right loop:


$$-V_s - 5 + 4V_x = 0$$

$$-V_s - 5 + 4(2) = 0$$

$$-V_s + 3 = 0$$

$$V_s = 3V$$

Find resistance of A:

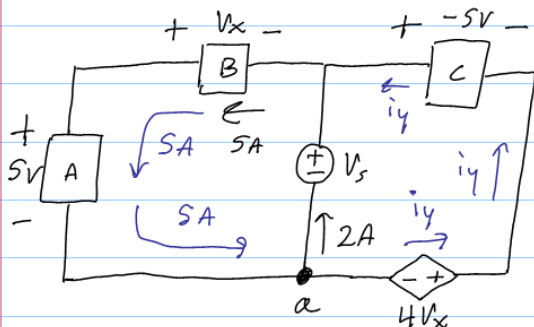

Passive sign, so,

Ohm's Law:  $R = \frac{V}{I}$

$$R_A = \frac{5}{5}$$

$$R_A = 1\Omega$$

Find  $P_{4V_x}$ :

KCL @ a:

$$-5 + 2 + i_y = 0 \quad \star \text{ I have defined } i_y \text{ here.}$$

$$-3 + i_y = 0$$

$$i_y = 3A$$

Voltage of dependent source:

$$4 \cdot V_x = 4 \cdot 2 = 8V$$



is not passive sign,  
so  $P = -v_i$ .

$$P_{4V_x} = -v_i = -8 \cdot 3$$

$$P_{4V_x} = -24W \text{ (delivering)}$$

$P < 0$ , so it is delivering power.

## Practice Exam 1 Question 2


Thursday, September 18, 2025

3:11 PM


Matthew

For the given circuit, use current division, voltage division, Ohm's Law, and the concept of equivalent resistance to find the following:

- a)  $V_s$
- b)  $V_1$
- c)  $I_2$

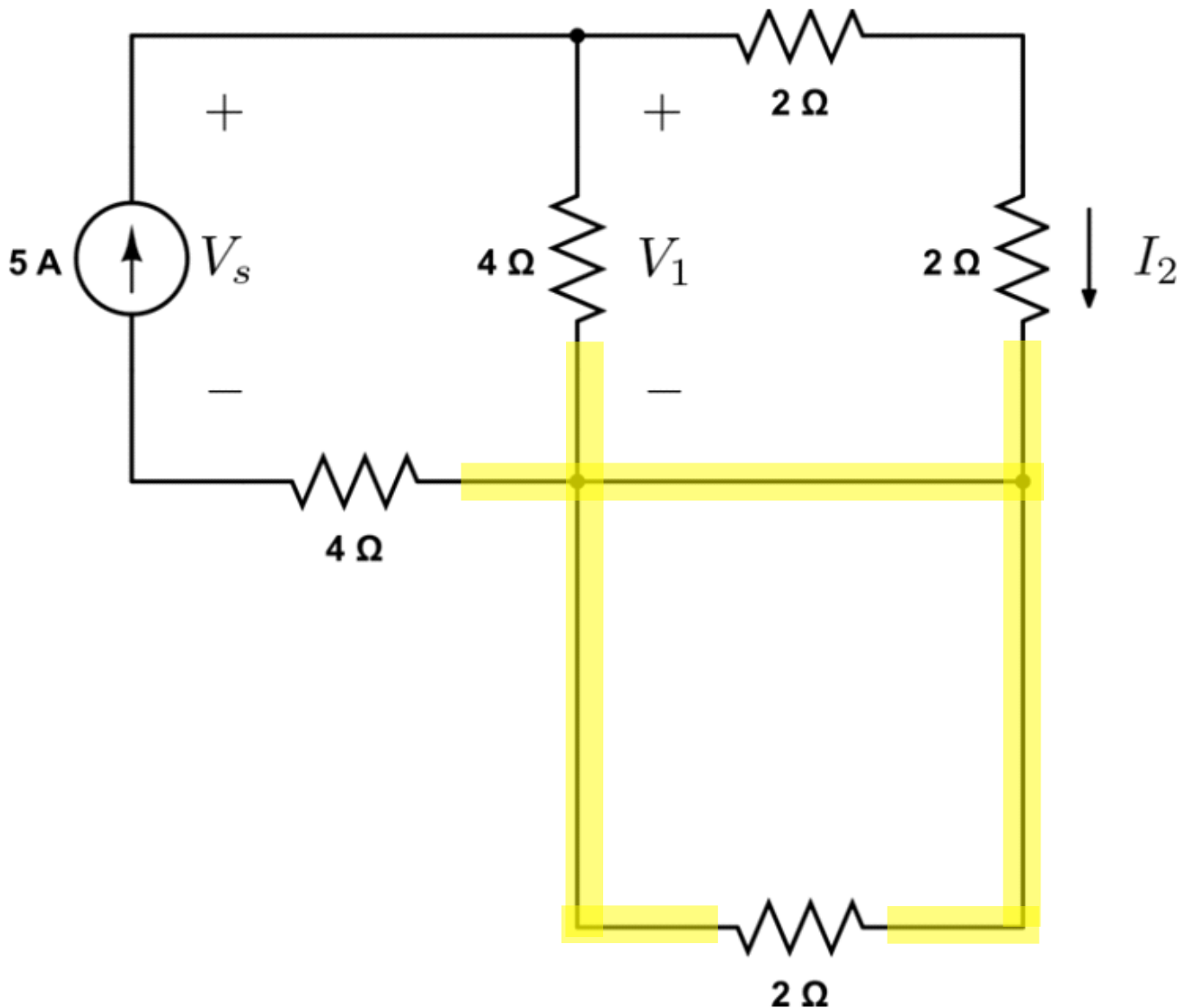

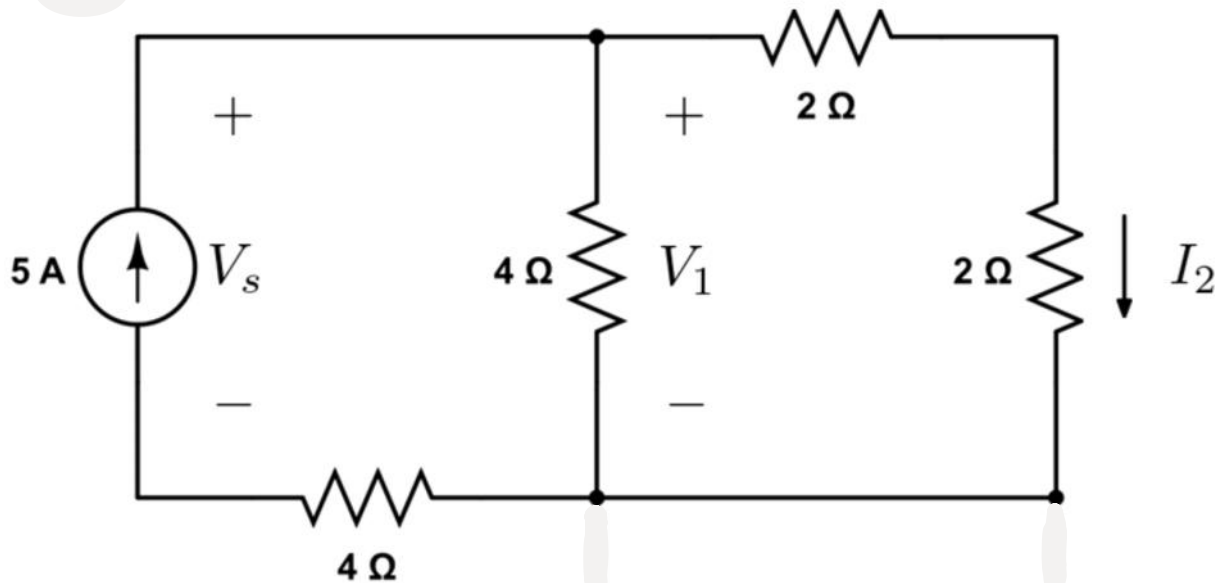
Both sides of the  $2\ \Omega$  resistor are connected to the same node, so it is shorted.



Equivalent Resistance seen by the source:


$$((2\Omega + 2\Omega) \parallel 4\Omega) + 4\Omega = 6\Omega$$

Equivalent Circuit:

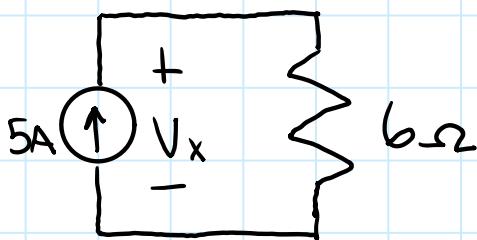

$$\text{KVL: } -V_x + 6(5A) = 0$$

$$V_x = 30V$$

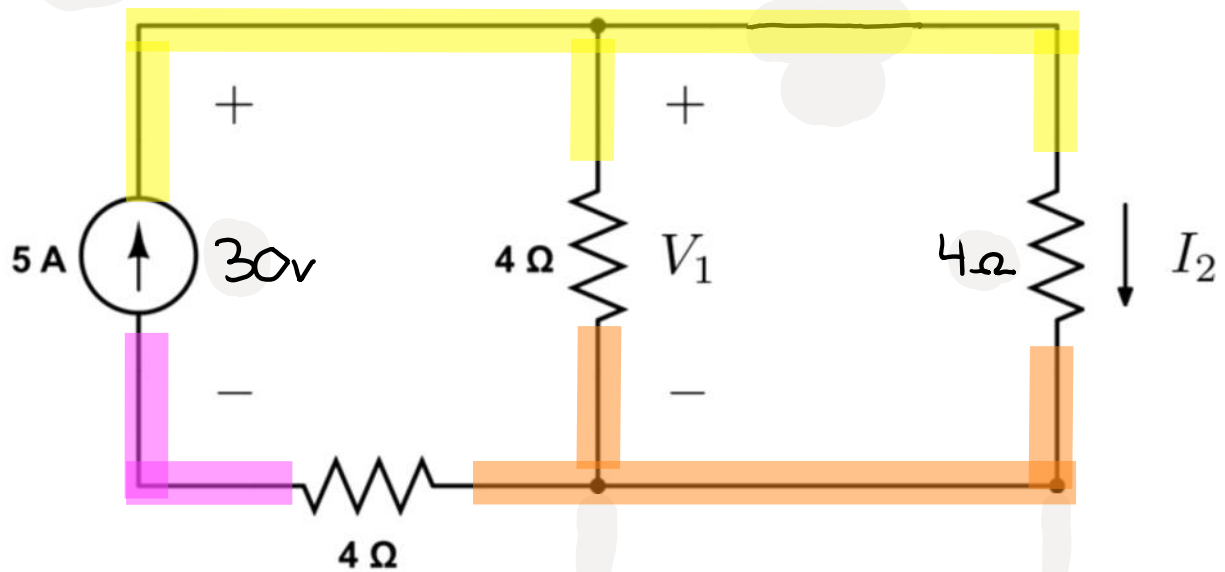

We can find  $V_1$  with Voltage Division

The right and middle resistor share  $V_1$  volts, but  $V_1 \neq 30\text{V}$

$$V_1 = \frac{(4\Omega || 4\Omega)}{6\Omega} \cdot 30\text{V} = 10\text{V}$$

We can find  $I_2$  with Current Division

$$I_2 = \frac{(4\Omega || 4\Omega)}{4\Omega} \cdot 5\text{A} = 2.5\text{A}$$


Equivalent Resistance for Current Division  
is for parallel resistors only

Equivalent Resistance for Voltage Division  
is for series resistors only

$$V_s = 30\text{v}$$

$$V_1 = 10\text{v}$$

$$I_2 = 2.5\text{A}$$

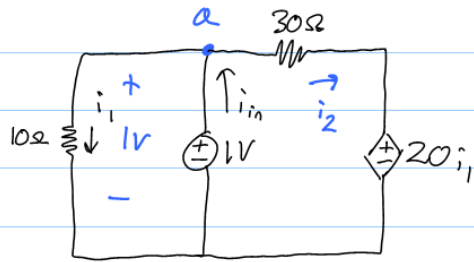

Find  $R_{eq}$  seen by 1V source.  
For:

$$R_{eq} = \frac{V_s}{i_s} \quad V_s = 1, \text{ so } R_{eq} = \frac{1}{i_s}$$

so,  $R_{eq} = \frac{1}{i_{in}}$

10Ω resistor is in parallel with 1V source.

$$i_1 = \frac{V}{R} = \frac{1}{10} \text{ A} = 0.1 \text{ A}$$

KVL right loop:

$$-1 + 30i_2 + 20i_1 = 0$$

$$-1 + 30i_2 + 20(0.1) = 0$$

$$-1 + 30i_2 + 2 = 0$$

$$30i_2 = -1$$

$$i_2 = -\frac{1}{30} \text{ A}$$

KCL @ a:

$$i_1 - i_{in} + i_2 = 0$$

$$\frac{1}{10} - i_{in} + \left(-\frac{1}{30}\right) = 0$$

$$\frac{1}{15} - i_{in} = 0$$

$$i_{in} = \frac{1}{15} \text{ A}$$

$$R_{eq} = \frac{1}{i_{in}} = \frac{1}{\frac{1}{15}} \Omega$$

$$R_{eq} = 15 \Omega$$