


Linear Circuits One (EEL 3004C)

Practice Exam 2

Matthew Giannacco

For the given circuit, use mesh analysis to find the following:


- Every single node voltage
- I_o

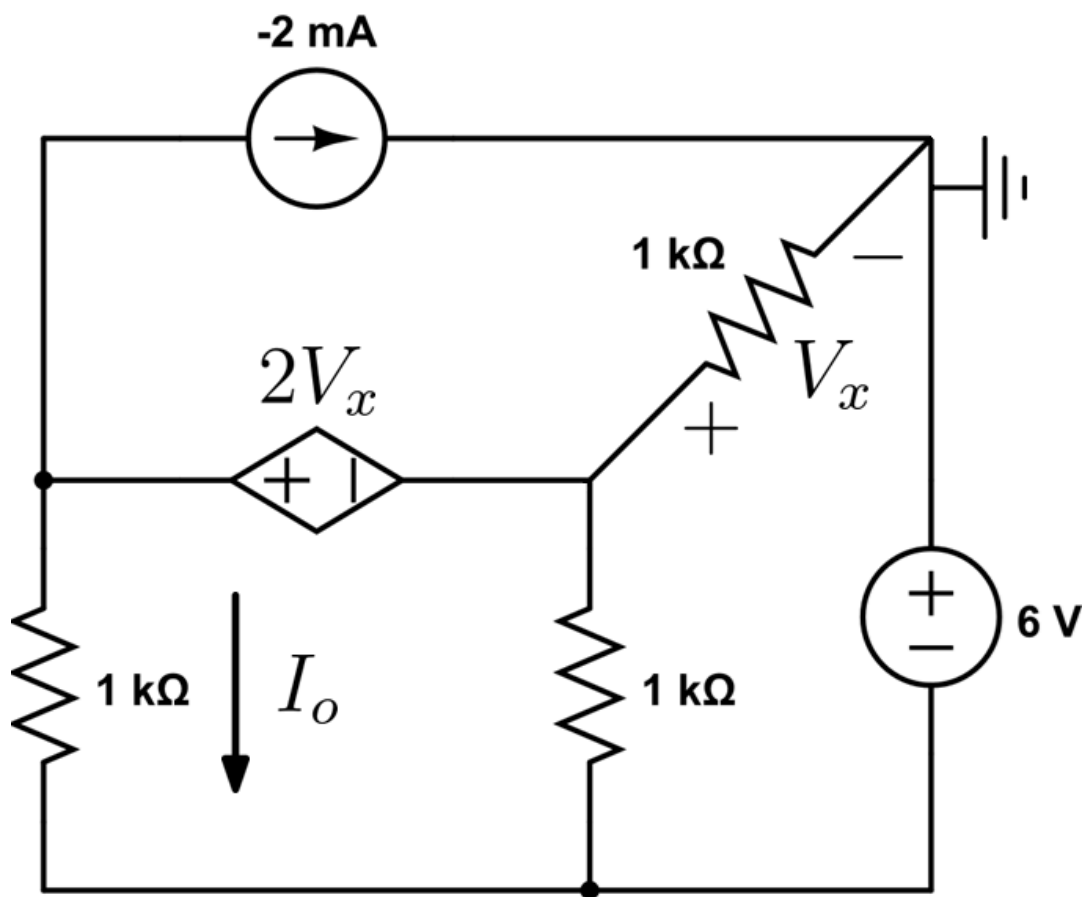

For the given circuit, use mesh analysis to find the following:

a) Every single mesh current (assume clockwise direction)

b) V_y

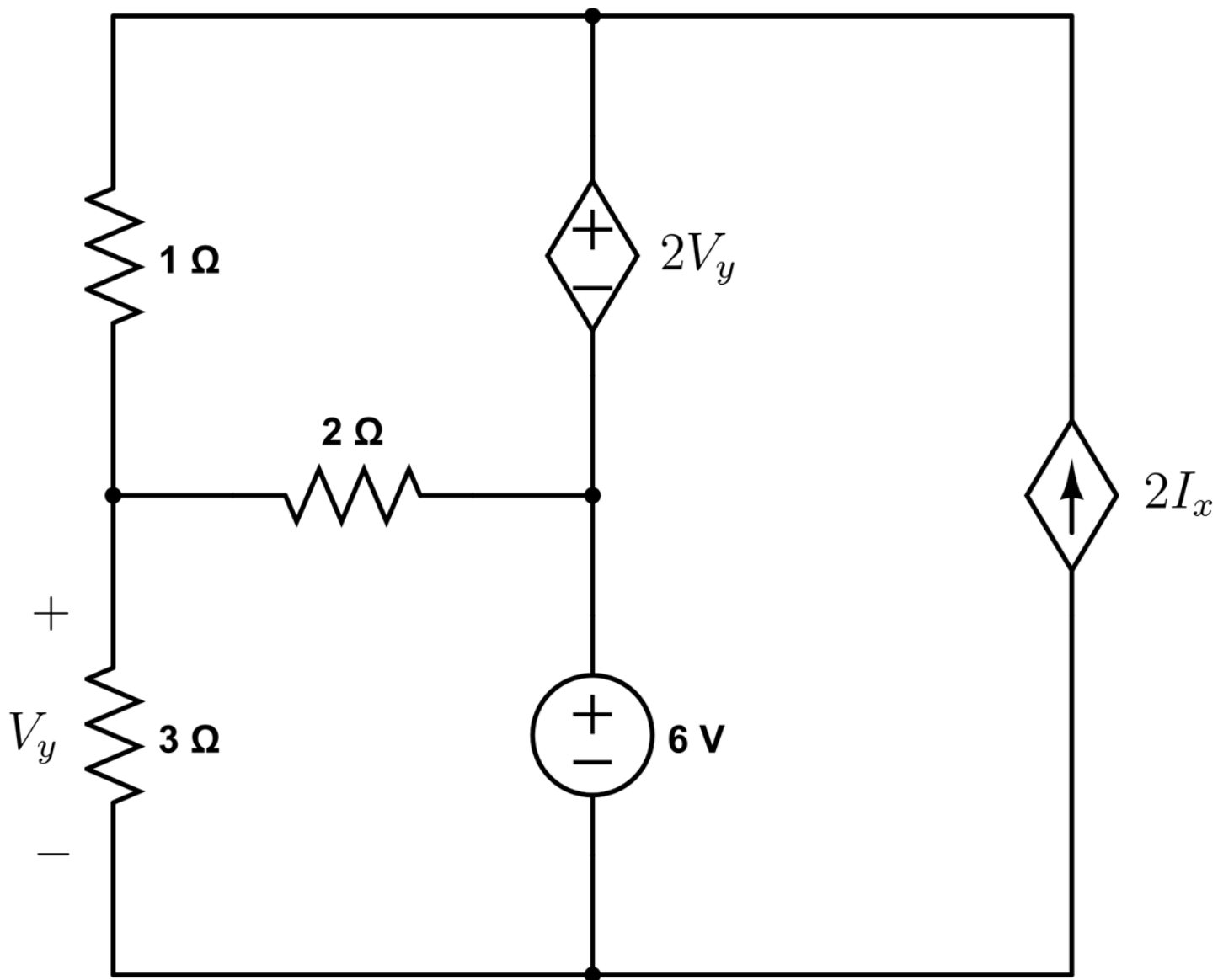

For the given circuit, find the following:

- The Thevenin equivalent circuit seen from a to b
- The Norton equivalent circuit seen from a to b
- The maximum power that could be dissipated in a load resistor R_L connected between a and b

