


Practice Quiz One Solution: KCL, KVL, and Ohm's Law (Intermediate)

For the circuit shown below, with an unknown circuit element, find the following:

- a) v_x
- b) i_x
- c) R_x
- d) i_y

Finally, calculate the power of the unknown circuit element and state whether the power is absorbed or delivered.

Step One: KVL, right loop, following 1A:

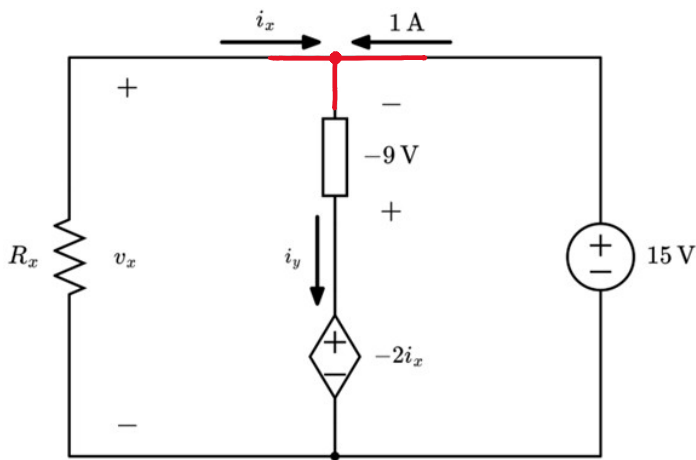

$$\begin{aligned} -(-9) + (-2i_x) - 15 &= 0 \\ -2i_x &= 6 \\ i_x &= -3\text{A} \end{aligned}$$

Step Two: KVL, left loop, following i_x :

$$-(-9) + (-2i_x) - V_x = 0 \quad i_x = -3\text{A}$$

$$V_x = 15\text{V}$$

Also, you can identify that the Independent Voltage Source is in parallel with V_x


Step Three: Ohm's Law, observing passive sign convention:

$$R_x = -\frac{V_x}{i_x} = -\frac{15\text{V}}{-3\text{A}} = 5\Omega$$

Step Four: KCL, highlighted node:

$$\begin{aligned} -i_x - 1 + i_y &= 0 \\ i_y &= -2\text{A} \end{aligned}$$

Step Five: Power Calculation

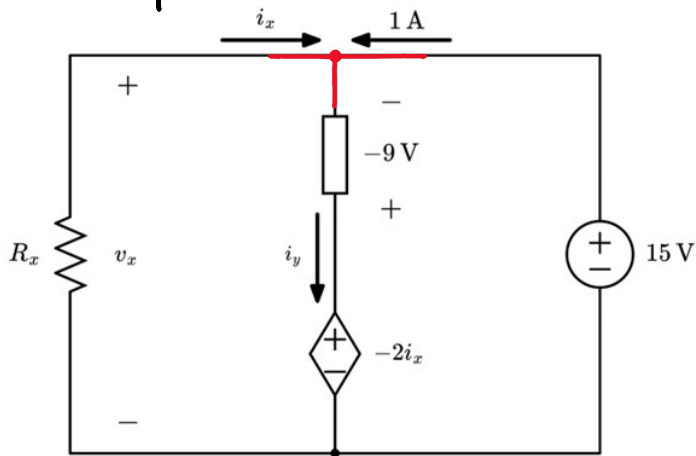

$$P_{\text{element}} = (-9\text{V}) \cdot (-(-2\text{A}))$$

$$P_{\text{element}} = -18\text{W} \text{ Delivering}$$

Self-Grading Rubric

Correct KVL equation for the right loop	+1.5 points
Correct value for i_x	+1.5 point
Identify $v_x = 15\text{ V}$, either using a KVL equation or by inspection	+1.5 point
Correct value for i_y using a KCL equation	+1.5 points
Identify $R_x = 5\ \Omega$ by using Ohm's law and Passive Sign Convention (no credit for answering $R_x = -5\ \Omega$)	+1.5 point
Correct value for the power of the unknown element (P_{element})	+1.5 point
Correct sign for the power of the unknown element	+0.5 point
Mention that the unknown element is delivering power	+0.5 point