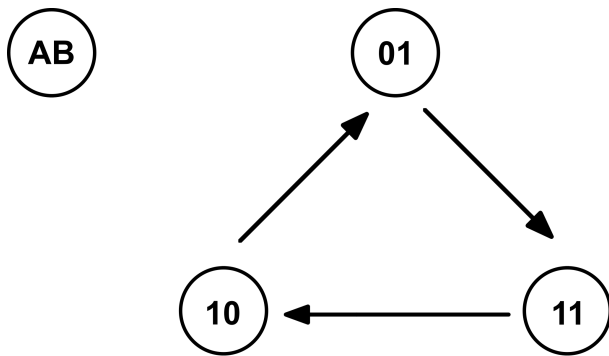


1. Using the state diagram, design and draw a T flip flop for A and a JK flip flop for B



Step 1: Draw a next-state table for AB

Step 2: Use K-maps to find T_A , J_B , and K_B

Step 3: Draw the digital circuit