

Practice Quiz Three: Superposition (Intermediate)

For the circuit shown below, use the principle of superposition to find v_o . Clearly redraw the circuit in each state.

Suggested time limit: 10 minutes

