

Practice Quiz Eight: RL and RC Circuits (Hard)

For the circuit shown below, find the following:

- The initial current $i_L(0)$.
- The steady-state expression for the inductor current $i_L(t)$ for $t \geq 0^+$.
- The steady-state expression for the resistor current $i_o(t)$ for $t \geq 0^+$.

Suggested time limit: 15 minutes

