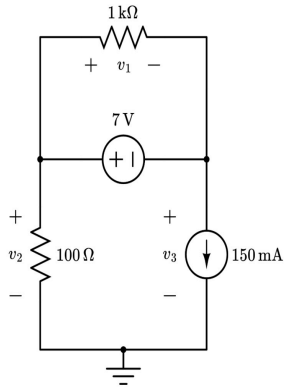


Practice Quiz Four: Node Voltage Analysis (Easy)

For the circuit shown below, use node voltage analysis to find the value of v_1 , v_2 , and v_3 .

Suggested time limit: 10 minutes



Step #1 Constraint

$$v_2 - v_3 = 7$$

$$v_1 = v_2 - v_3$$

Step #2 Supernode

$$\left(\frac{v_2 - 0}{100} + \frac{v_2 - v_3}{1000} + \frac{v_3 - v_2}{1000} + (150 \cdot 10^{-3}) = 0 \right) 1000$$

$$10v_2 + v_2 - v_3 + v_3 - v_2 + 150 = 0$$

$$10v_2 = -150$$

$$v_2 = -15V$$

Step # 3 Solve

$$-15 - V_3 = 7$$

$$V_3 = -22V$$

$$V_1 = -15 - (-22)$$

$$V_1 = 7V$$