

Practice Quiz One: KCL, KVL, and Ohm's Law (Easy)

For the circuit shown below, find the following:

- a) v_1
- b) i_1

Finally, calculate the power of the current-dependent current source and state whether the power is absorbed or delivered.

Suggested time limit: 10 minutes

