

## Practice Quiz One: KCL, KVL, and Ohm's Law (Intermediate)

For the circuit shown below, with an unknown circuit element, find the following:

- a)  $v_x$
- b)  $i_x$
- c)  $R_x$
- d)  $i_y$

Finally, calculate the power of the unknown circuit element and state whether the power is absorbed or delivered.

*Suggested time limit: 15 minutes*

