

Practice Quiz Ten: Phasors: Equivalent Impedance (Easy)

For the circuit shown below, find $i_s(t)$.

Suggested time limit: 10 minutes

$$v_s(t) = 20 \cos(100t + 30^\circ) \text{ V}$$

