

Practice Quiz Ten: Phasors: Equivalent Impedance (Intermediate)

For the circuit shown below, find $v_x(t)$ and $i_x(t)$.

Suggested time limit: 10 minutes

$$v_s(t) = 4\sqrt{2} \cos(2,000t - 60^\circ) \text{ V}$$

