

Practice Quiz Eleven: Complex Power Calculation (Hard)

For the circuit shown below, find the following:

- Average power P . Determine whether the power is absorbed or delivered.
- Reactive power Q . Determine whether the power is absorbed or delivered.

Finally, write an expression for the sum of average power (ΣP) and reactive power (ΣQ) for every element to check the balance between absorbed and delivered power.

Suggested time limit: 90 minutes

