

Practice Quiz Two: Equivalent Resistance (Easy)

For the circuit shown below, find the equivalent resistance R_{ab} .

Suggested time limit: 5 minutes

