

Practice Quiz Two: Equivalent Resistance (Hard)

For the circuit shown below, where every resistor has an identical resistance R , find the equivalent resistance R_{ab} seen by the independent current source. Express your answer in terms of R .

Suggested time limit: 15 minutes



