

### Practice Quiz Three: Superposition (Easy)

For the circuit shown below, use the principle of superposition to find  $i_o$ . Clearly redraw the circuit in each state.

*Suggested time limit: 10 minutes*

