

Practice Quiz Four: Node Voltage Analysis (Easy)

For the circuit shown below, use node voltage analysis to find the value of v_1 , v_2 , and v_3 .

Suggested time limit: 10 minutes

