

Practice Quiz Four: Node Voltage Analysis (Hard)

For the circuit shown below, use node voltage analysis to find the value of v_x .

Suggested time limit: 15 minutes

