

Practice Quiz Five: Mesh Current Analysis (Hard)

For the circuit shown below, use mesh current analysis to determine the value of both dependent sources. Your solution must explicitly define and solve for each mesh current.

Suggested time limit: 15 minutes

