

Practice Quiz Six: Thévenin and Norton Equivalent Circuits with Maximum Power Transfer (Easy)

For the circuit shown below:

- Find the Thévenin equivalent circuit with respect to the open terminal pair ab and clearly illustrate the equivalent circuit with every value labeled.
- If a load is connected to points a and b , what is the maximum power that can be delivered to a load resistor R_L ?

Suggested time limit: 10 minutes

