

Practice Quiz Six: Thévenin and Norton Equivalent Circuits with Maximum Power Transfer (Intermediate)

For the circuit shown below:

- Find the Thévenin equivalent circuit with respect to the open terminal pair ab .
- Find the Norton equivalent circuit with respect to the open terminal pair ab .
- Clearly illustrate both equivalent circuits with every value labeled.
- If a load is connected to points a and b , what is the maximum power that can be delivered to a load resistor R_L ?
- Determine the value of the load resistor R_L necessary to achieve maximum power transfer.

Suggested time limit: 20 minutes

