

## Practice Quiz Seven: RLC Circuit Analysis under DC Conditions (Easy)

For the RLC circuit at steady state shown below, find the following:

- a)  $v_1$
- b)  $v_2$
- c)  $i_1$
- d)  $i_2$

Finally, find the energy stored in both the inductor and the capacitor.

*Suggested time limit: 10 minutes*

