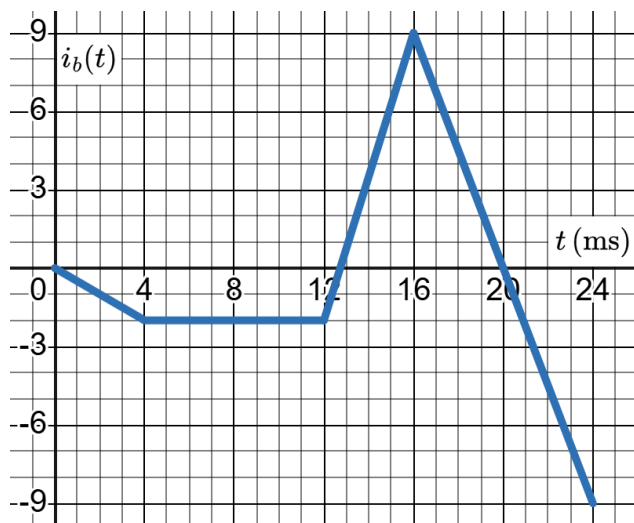


Practice Quiz Seven: Capacitance and Inductance (Intermediate)

For the inductive network shown below, connected to a black box, the following current waveform is given:



Sketch the waveform for $v_b(t)$ and $P_b(t)$.

Suggested time limit: 15 minutes

