

Practice Quiz Eight: RL and RC Circuits (Intermediate)

For the circuit shown below, find the steady-state expression for capacitor voltage, $v_c(t)$ for $t \geq 0^+$.

Suggested time limit: 10 minutes