

Practice Quiz Nine: Phasors: Equivalent Impedance (Easy)

For the circuit shown below, find the following:

- The phasor equivalent for the value of the voltage source, in polar form.
- The equivalent impedance seen by the source in both rectangular and polar form.
- The steady-state current $i_s(t)$, in polar form.

$$v_s(t) = 3 \cos(1,000t - 30^\circ) \text{ V}$$

Suggested time limit: 10 minutes

