

Practice Quiz Nine: Phasors: Equivalent Impedance (Intermediate)

For the circuit shown below, find $v_1(t)$ and $i_1(t)$.

Suggested time limit: 10 minutes

